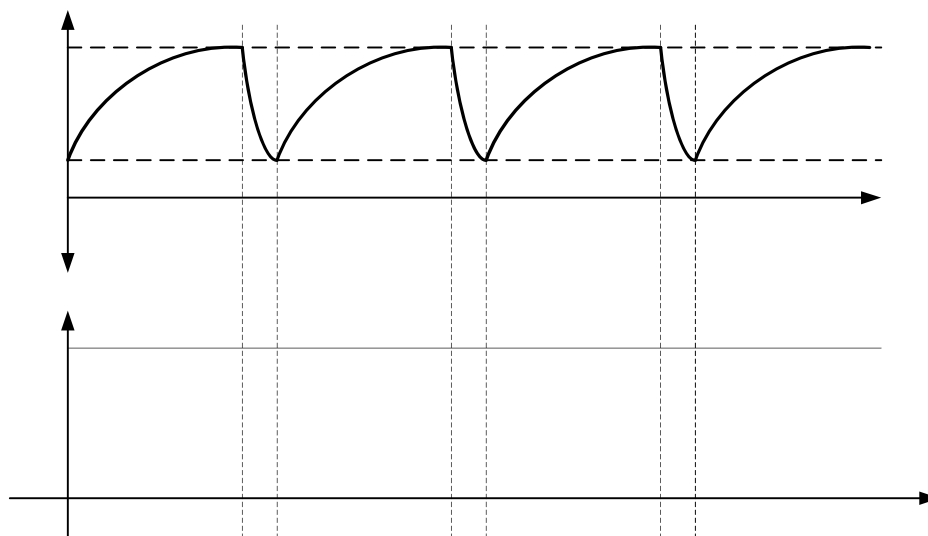


CENTRE NUMBER:							
----------------	--	--	--	--	--	--	--

EXAMINATION NUMBER:													
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET**QUESTION 4: SEMICONDUCTOR DEVICES**

4.3.4


**FIGURE 4.3.4**Transfer mark to
answer book

MOD

(3)

CENTRE NUMBER:**EXAMINATION NUMBER:****ANSWER SHEET**

4.5.2

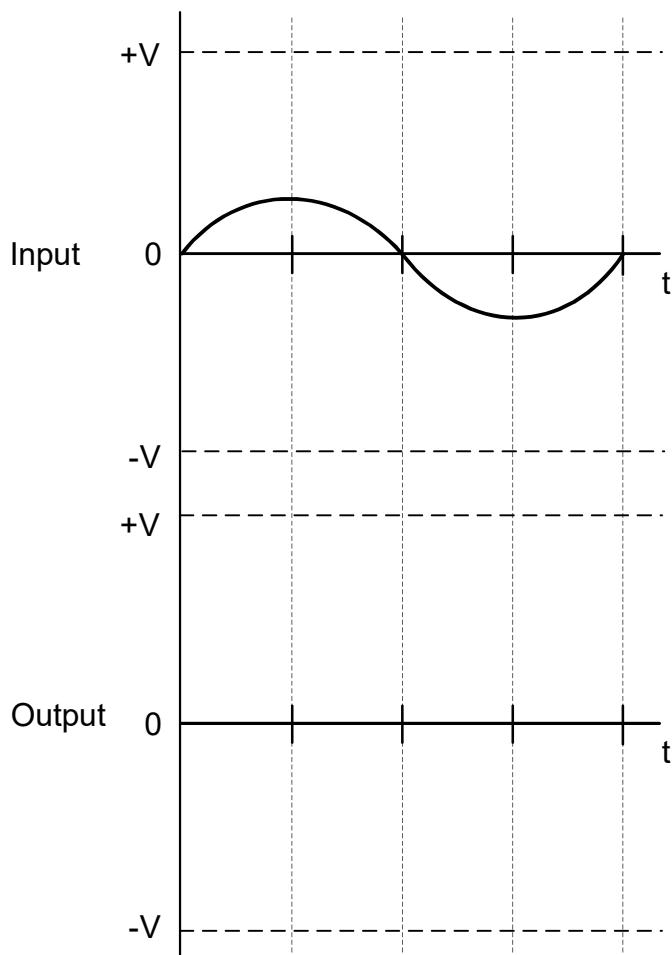Transfer mark to
answer book

MOD

FIGURE 4.5.2

(2)




CENTRE NUMBER:							
----------------	--	--	--	--	--	--	--

EXAMINATION NUMBER:													
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET**QUESTION 5: SWITCHING CIRCUITS**

5.1.6

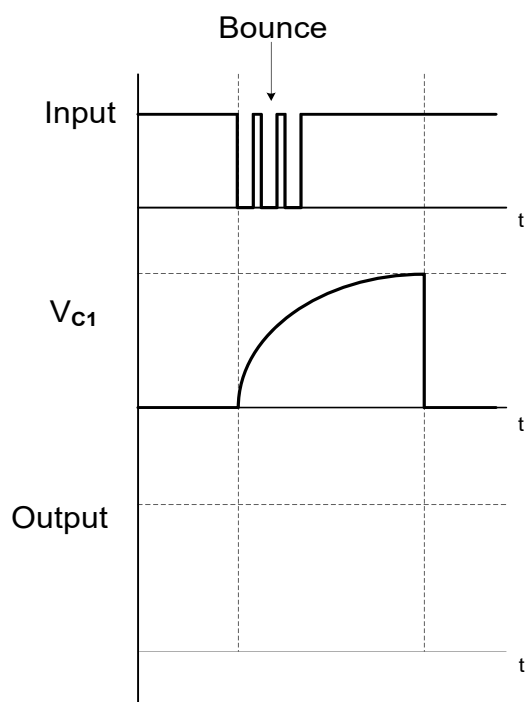**FIGURE 5.1.6**Transfer mark to
answer book

MOD

(3)



CENTRE NUMBER:

EXAMINATION NUMBER:

ANSWER SHEET

5.5.2

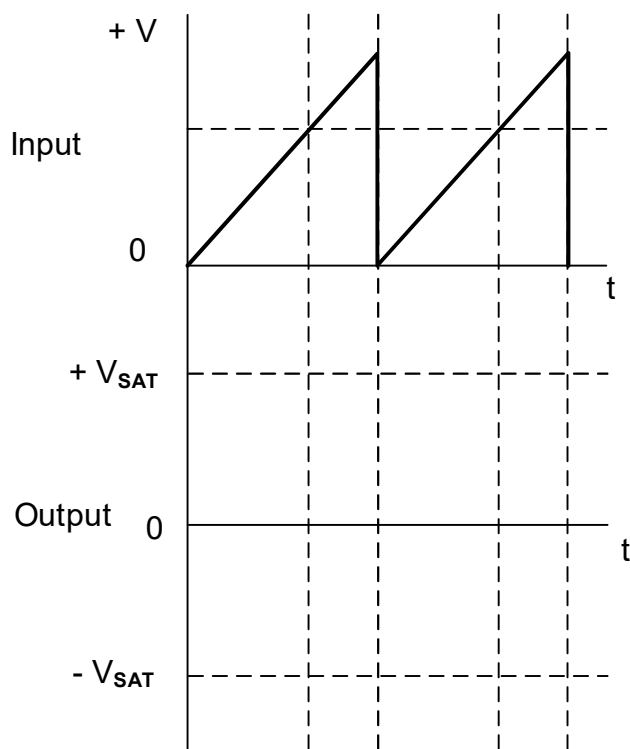


FIGURE 5.5.2

Transfer mark to
answer book

MOD

(3)

5.6.2

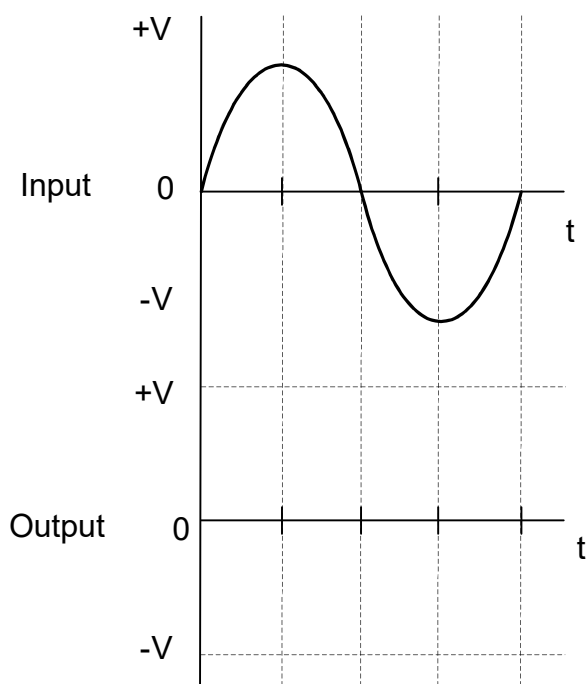


FIGURE 5.6.2

Transfer mark to
answer book

MOD

(4)




CENTRE NUMBER:							
----------------	--	--	--	--	--	--	--

EXAMINATION NUMBER:													
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET**QUESTION 6: AMPLIFIERS**

6.3.3

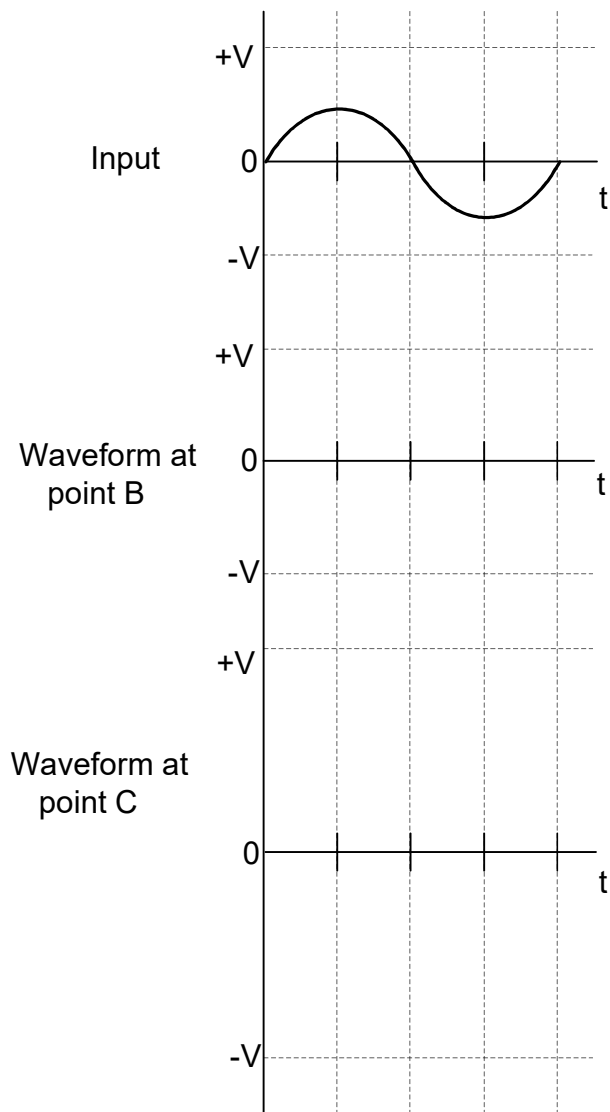Transfer mark to
answer book

MOD

FIGURE 6.3.3**(4)**